



SATHYABAMA

INSTITUTE OF SCIENCE AND TECHNOLOGY
(DEEMED TO BE UNIVERSITY)

Accredited with 'A' Grade by NAAC



Lecture session 5_ UNIT-3_Continuation

Unit-3-COMBINATIONAL LOGIC

CODE CONVERSION

By

V.GEETHA

ASSISTANT PROFESSOR/EEE

SATHYABAMA INSTITUTE OF SCIENCE AND TECHNOLOGY

CHENNAI-119

Code Converter

Binary to Gray Code Converter


The Gray Code is unweighted and is not an arithmetic code: that is, there are no specific weights assigned to the bit positions. The important feature of the Gray Code is that it exhibits only a single bit change from one code word to the next in sequence. This property is important in many applications, such as shaft position encoders, where error susceptibility increases with the number of bit changes between adjacent numbers in a sequence.

To convert a binary number to a Gray Code number, the following rules apply.

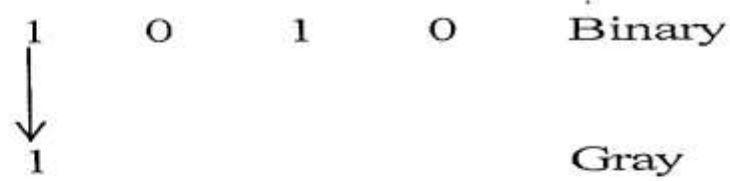
1. The most significant digit (Left Most Bit) in the Gray Code is the same as the corresponding digit in the binary number.
2. Going from left to right, add each adjacent pair of binary digits to get the next Gray code digit, regardless carries.

For instance - Let us convert the binary number 1010 to Gray Code.


Step 1 - The left most Gray digit is the same as the left most binary



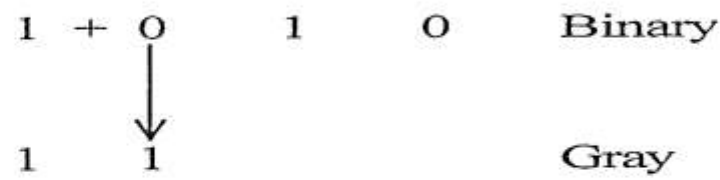
Step 2 - Add the left most binary digit to the adjacent one.



Step 3 - Add the next adjacent pair

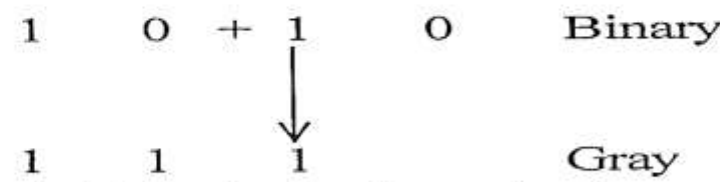

Step 4 -Add the last adjacent pair

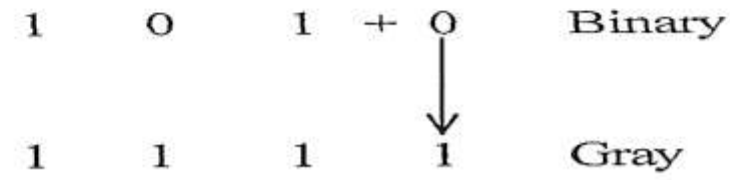

The conversion is now complete and the Gray Code is 1111.

Steps to design the converter

1. Design a converter by the following procedures:
 - a. Write down the truth table of both input and output bits of the converter.
 - b. Apply Karnaugh Map to look for the minimized logic expression for the output bits.
 - c. Implement the logic gates by using Circuit

Maker. Example:

For Binary to Gray Code Converter, binary bits are input and gray code bits are output. So first write the truth table for binary bits and gray code. Then k-map for the all bits of gray code, find the simplified expression for each bit of gray code. Then design the logical circuit.

Truth Table

| Natural-binary code | | | | Gray code | | | |
|---------------------|----|----|----|-----------|----|----|----|
| B3 | B2 | B1 | B0 | G3 | G2 | G1 | G0 |
| | | | | | | | |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |

K-Map for each bit of Gray code

K-map for G_0

| | | | | | |
|-----------|----|----|----|----|----|
| $B_1 B_0$ | | | | | |
| | | 00 | 01 | 11 | 10 |
| $B_2 B_1$ | 00 | 0 | 1 | 0 | 1 |
| | 01 | 0 | 1 | 0 | 1 |
| | 11 | 0 | 1 | 0 | 1 |
| | 10 | 0 | 1 | 0 | 1 |

$$G_0 = B_1' B_0 + B_1 B_0'$$

$$G_0 = B_0 \oplus B_1$$

K-map for G_1

| | | | | | |
|-----------|----|----|----|----|----|
| $B_1 B_0$ | | | | | |
| | | 00 | 01 | 11 | 10 |
| $B_2 B_1$ | 00 | 0 | 0 | 1 | 1 |
| | 01 | 1 | 1 | 0 | 0 |
| | 11 | 1 | 1 | 0 | 0 |
| | 10 | 0 | 0 | 1 | 1 |

$$G_1 = B_1' B_2 + B_1 B_2'$$

$$G_2 = B_1 \oplus B_2$$

K-map for G_2


| $B_1 B_0$ | | 00 | 01 | 11 | 10 |
|-----------|----|----|----|----|----|
| $B_3 B_2$ | 00 | 0 | 0 | 0 | 0 |
| | 01 | 1 | 1 | 1 | 1 |
| | 11 | 0 | 0 | 0 | 0 |
| | 10 | 1 | 1 | 1 | 1 |

And
 $G_3 = B_3$

$$G_2 = B'_3 B_2 + B_3 B'_2$$

$$G_2 = B_2 \oplus B_3$$

Binary to Gray Converter

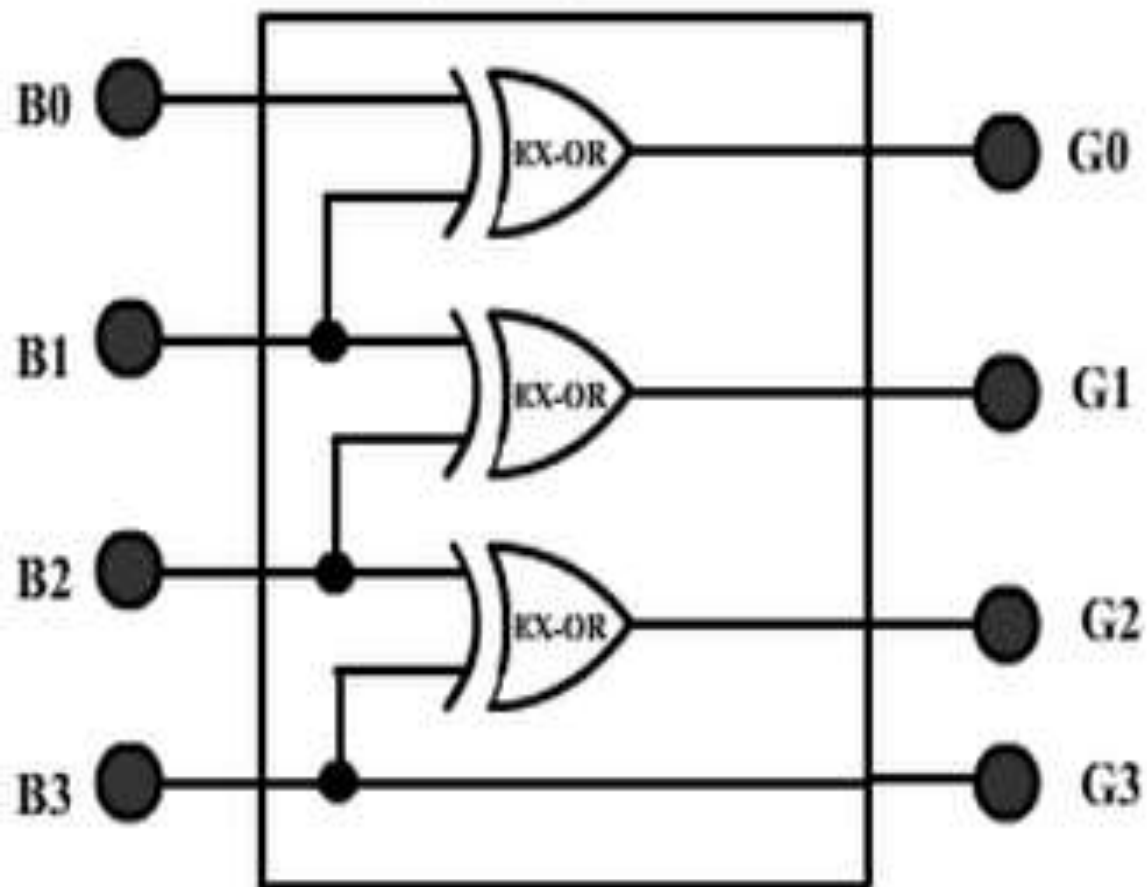

Gray to Binary Converter

Truth Table

| Gray code | | | | Natural-binary code | | | |
|-----------|----|----|----|---------------------|----|----|----|
| G3 | G2 | G1 | G0 | B3 | B2 | B1 | B0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |

K-map for B_0

| | | | | | |
|-------------------|--|----|----|----|----|
| $G_2 \ G_1 \ G_0$ | | | | | |
| | | 00 | 01 | 11 | 10 |
| 00 | | 0 | 1 | 0 | 1 |
| 01 | | 1 | 0 | 1 | 0 |
| 11 | | 1 | 0 | 1 | 0 |
| 10 | | 0 | 1 | 0 | 1 |

$$\begin{aligned}
 B_0 &= G_2 G_1' G_0' + G_2' G_1 G_0' + G_2' G_1' G_0 + G_2 G_1 G_0 \\
 &= G_0' (G_1' G_2 + G_1 G_2') + G_0 (G_1 G_2 + G_1' G_2') \\
 &= G_0' (G_2 \oplus G_1) + G_0 (G_2 \oplus G_1)' = G_0 \oplus G_1 \oplus G_2
 \end{aligned}$$

K-map for B_1

| | | | | | |
|-------------|--|----|----|----|----|
| $G_3 \ G_2$ | | | | | |
| | | 00 | 01 | 11 | 10 |
| 00 | | 0 | 0 | 1 | 1 |
| 01 | | 1 | 1 | 0 | 0 |
| 11 | | 0 | 0 | 1 | 1 |
| 10 | | 1 | 1 | 0 | 0 |

$$\begin{aligned}
 B_1 &= G_3' G_2' G_1 + G_3' G_2 G_1' + G_3 G_2 G_1 + G_3 G_2' G_1' \\
 &= G_3' (G_2 \oplus G_1) + G_3 (G_2 \oplus G_1)' \\
 &= G_1 \oplus G_2 \oplus G_3
 \end{aligned}$$

K-map for B₂


| $G_1 G_0$ $G_3 G_2$ | | | | | |
|------------------------|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| 00 | 0 | 0 | 0 | 0 | 0 |
| 01 | 1 | 1 | 1 | 1 | 1 |
| 11 | 0 | 0 | 0 | 0 | 0 |
| 10 | 1 | 1 | 1 | 1 | 1 |

$$\begin{aligned}
 B_2 &= G_3' G_2 + G_3 G_2' \\
 &= G_3 \oplus G_2
 \end{aligned}$$

And

$$B_3 = G_3$$

Gray to Binary Converter

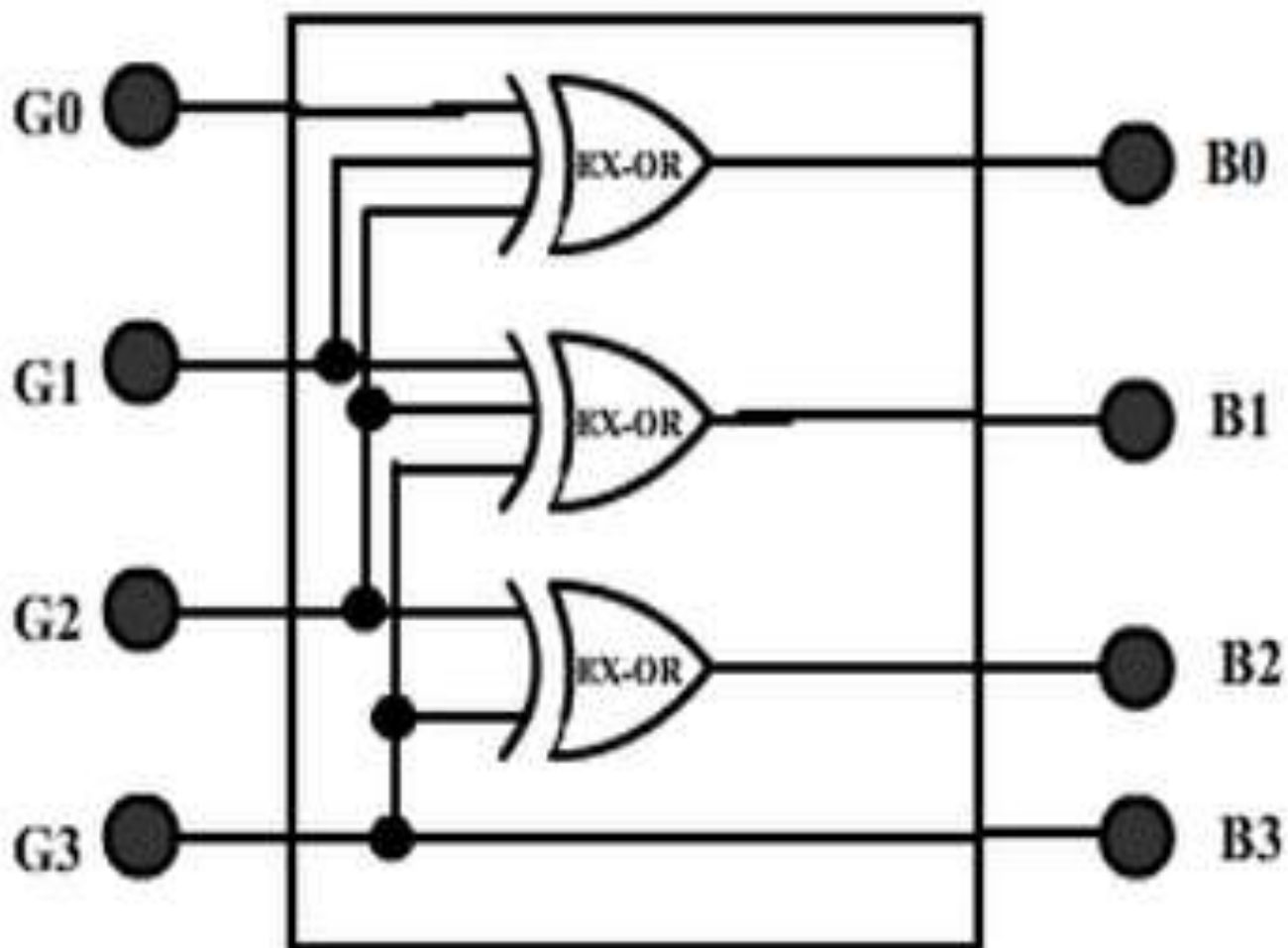

BCD TO EXCESS 3





As is clear by the name, a BCD digit can be converted to its corresponding Excess-3 code by simply adding 3 to it.


Let A , B , C , and D be the bits representing the binary numbers, where D is the LSB and A is the MSB, and

Let w , x , y , and z be the bits representing the gray code of the binary numbers, where z is the LSB and w is the MSB.

The truth table for the conversion is given below. The X's mark don't care conditions.

| BCD(8421) | | | | Excess-3 | | | |
|-----------|---|---|---|----------|---|---|---|
| A | B | C | D | w | x | y | z |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | X | X | X | X |
| 1 | 0 | 1 | 1 | X | X | X | X |
| 1 | 1 | 0 | 0 | X | X | X | X |
| 1 | 1 | 0 | 1 | X | X | X | X |
| 1 | 1 | 1 | 0 | X | X | X | X |
| 1 | 1 | 1 | 1 | X | X | X | X |

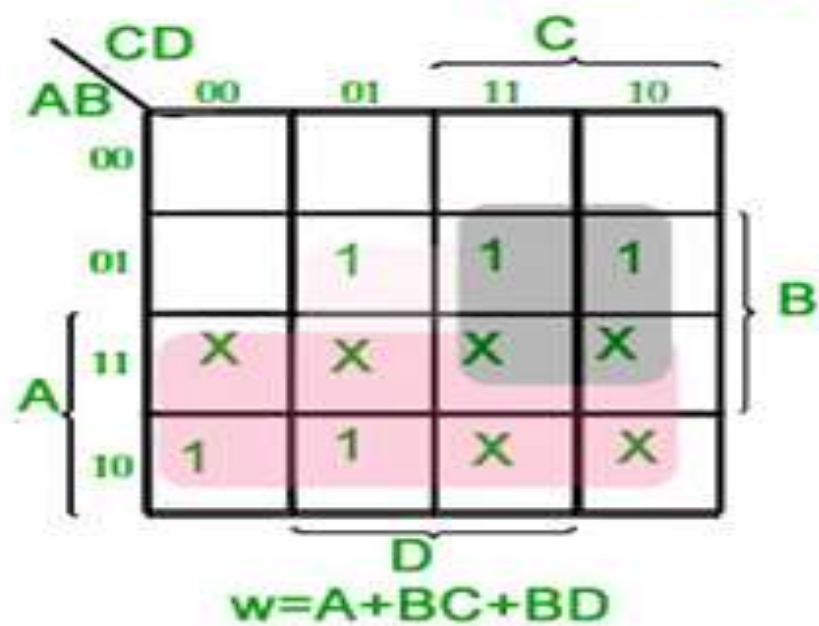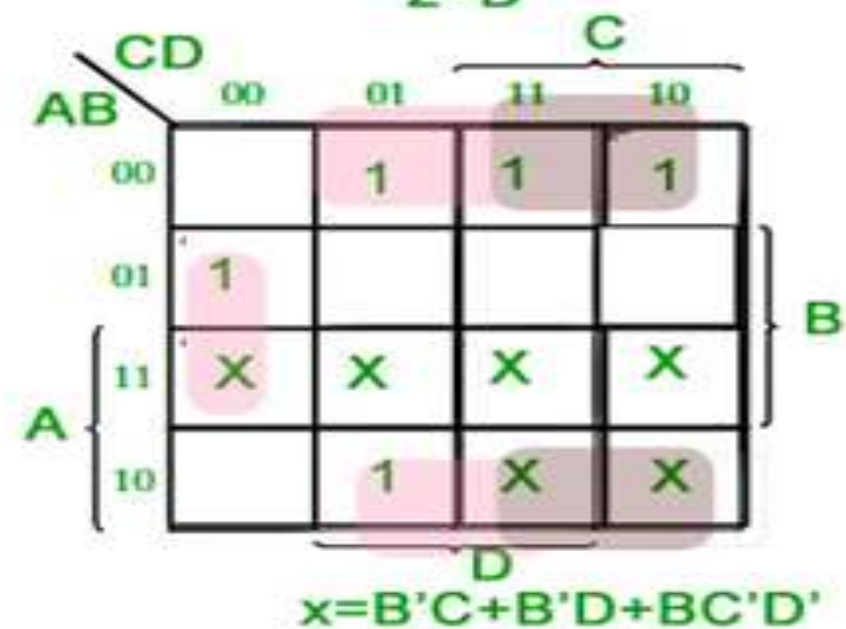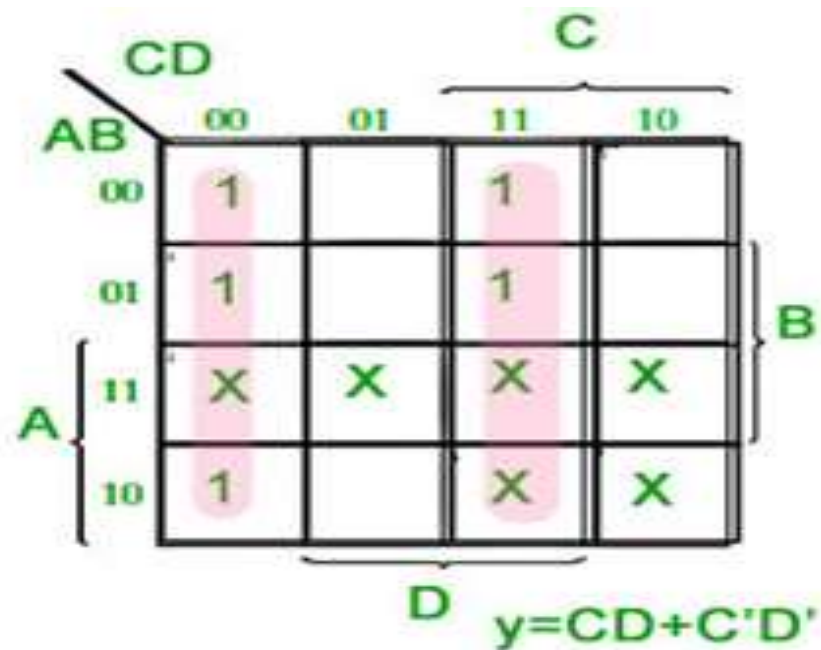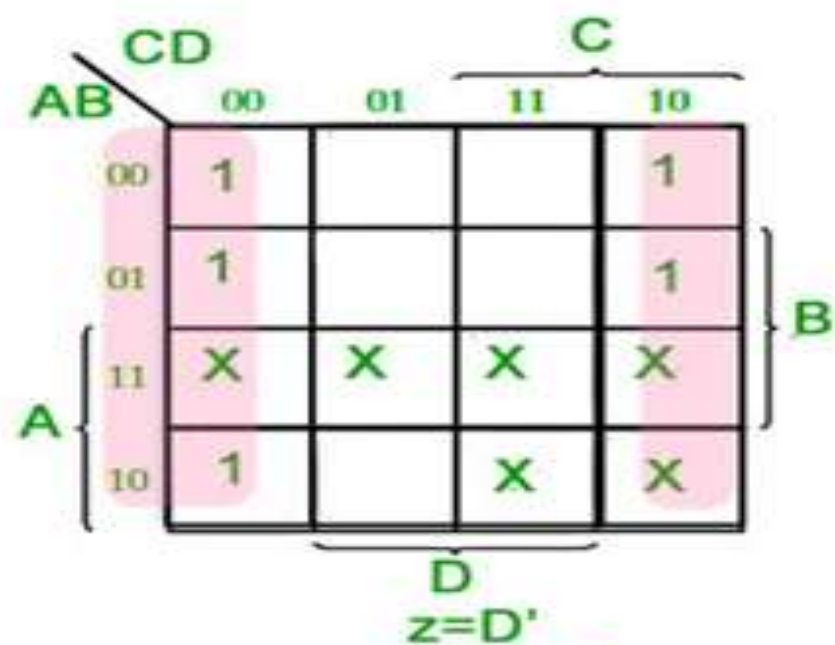

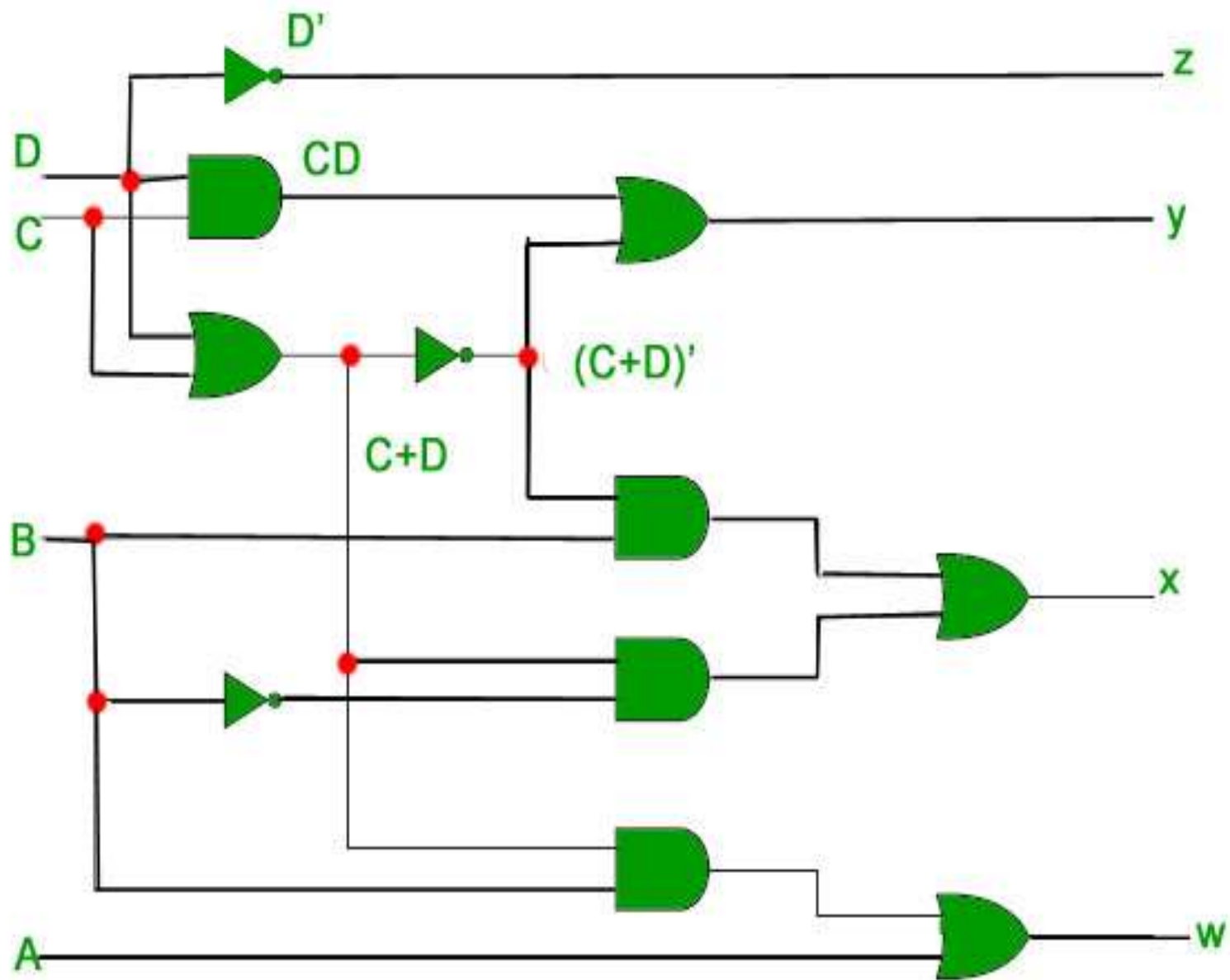

BCD TO SEVEN SEGMENT DISPLAY

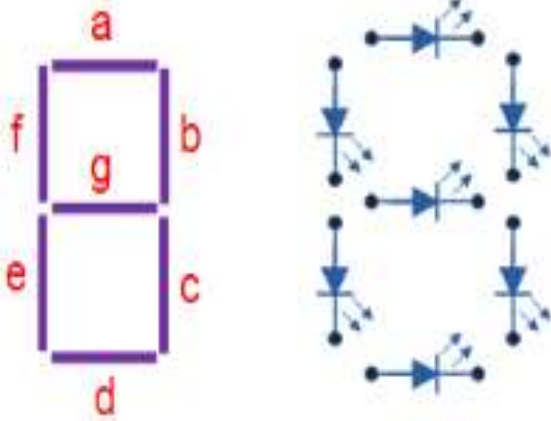


Figure1 Seven segment display

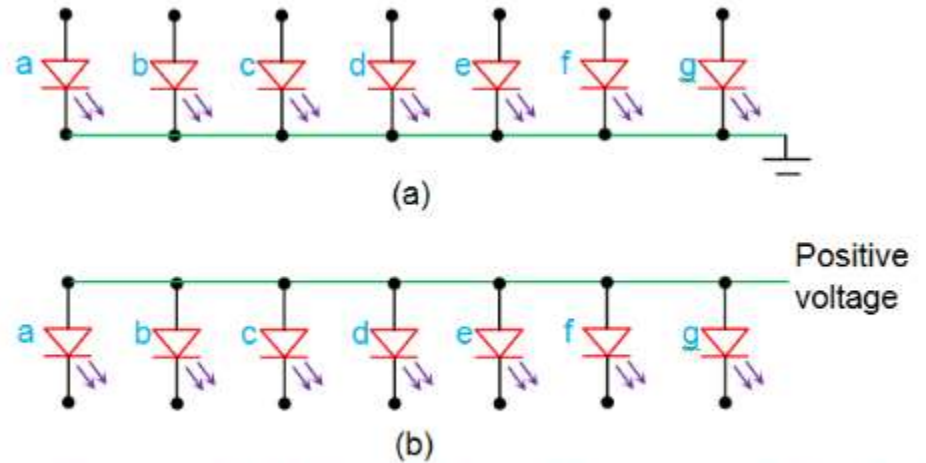


Figure 2 (a) Common cathode type display (b) Common anode type display



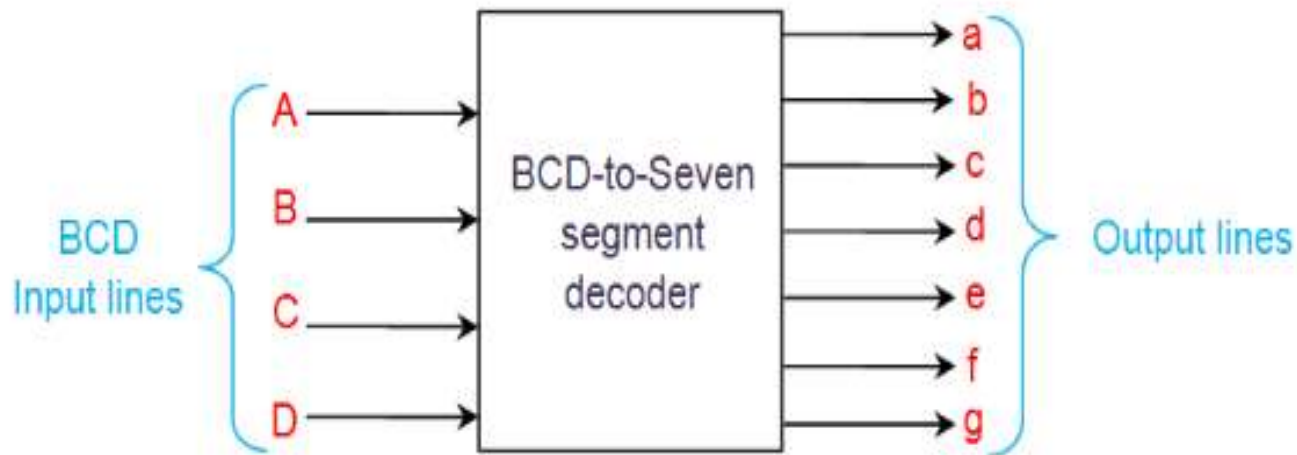
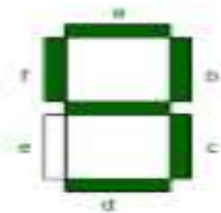
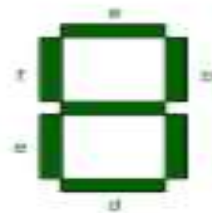
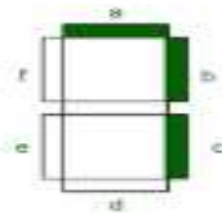
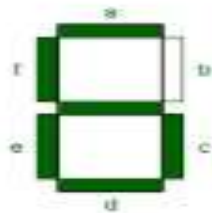
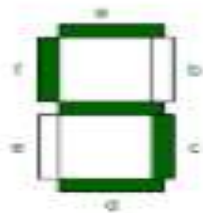
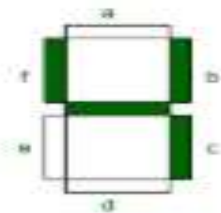
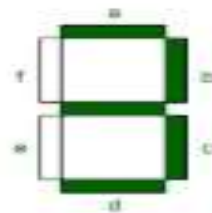
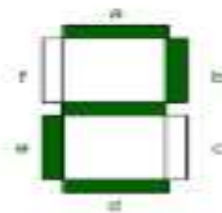
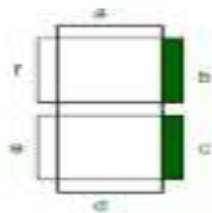


Figure 3 BCD-to-Seven segment decoder

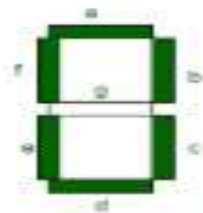

| Decimal Digit | Input lines | | | | Output lines | | | | | | | Display pattern |
|---------------|-------------|---|---|---|--------------|---|---|---|---|---|---|-----------------|
| | A | B | C | D | a | b | c | d | e | f | g | |
| 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 |
| 2 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 2 |
| 3 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 3 |
| 4 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 4 |
| 5 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 5 |
| 6 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 6 |
| 7 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 7 |
| 8 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 8 |
| 9 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 9 |

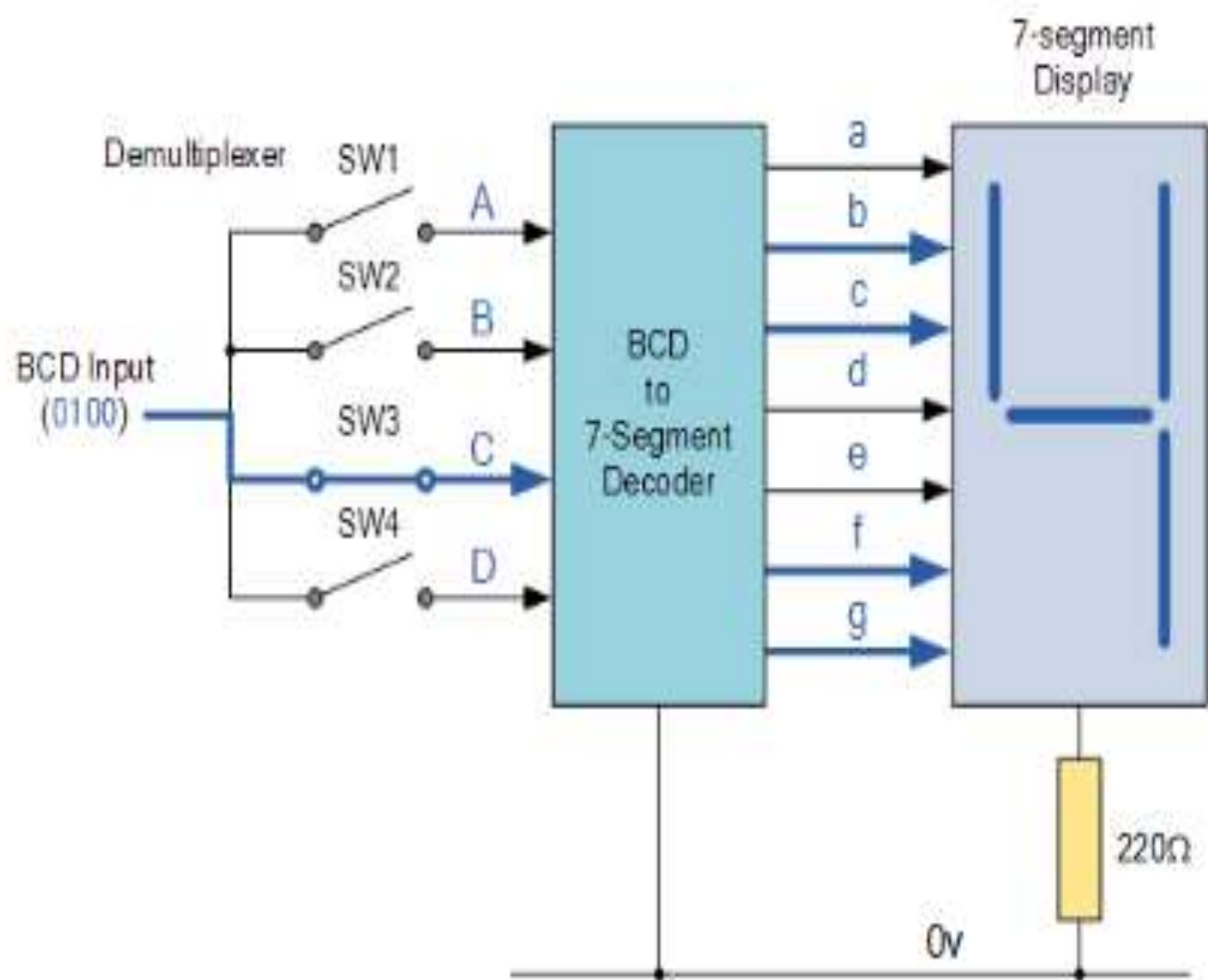

| AB\CD | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 00 | 1 | 0 | 1 | 1 |
| 01 | 0 | 1 | 1 | 1 |
| 11 | X | X | X | X |
| 10 | 1 | 1 | X | X |

FOR a: $F(A,B,C,D)=B'D'+C+BD+A$

| AB\CD | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 00 | 1 | 1 | 1 | 0 |
| 01 | 1 | 1 | 1 | 1 |
| 11 | X | X | X | X |
| 10 | 1 | 1 | X | X |

FOR c: $F(A,B,C,D)=C'+D+B$

| AB\CD | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 00 | 1 | 1 | 1 | 1 |
| 01 | 1 | 0 | 1 | 0 |
| 11 | X | X | X | X |
| 10 | 1 | 1 | X | X |

For b: $F(A,B,C,D)=B'+C'D'+CD$

| AB\CD | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 00 | 1 | 0 | 1 | 1 |
| 01 | 0 | 1 | 0 | 1 |
| 11 | X | X | X | X |
| 10 | 1 | 1 | X | X |

FOR d: $F(A,B,C,D)=B'D'+B'C+BC'D+CD'+A$

| AB\CD | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 00 | 1 | 0 | 0 | 1 |
| 01 | 0 | 0 | 0 | 1 |
| 11 | X | X | X | X |
| 10 | 1 | 0 | X | X |


FOR e: $F(A,B,C,D) = B'D' + CD'$

| AB\CD | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 00 | 1 | 0 | 0 | 0 |
| 01 | 1 | 1 | 0 | 1 |
| 11 | X | X | X | X |
| 10 | 1 | 1 | X | X |

FOR f: $F(A,B,C,D) = C'D' + BC' + BD' + A$

| AB\CD | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 00 | 0 | 0 | 1 | 1 |
| 01 | 1 | 1 | 0 | 1 |
| 11 | X | X | X | X |
| 10 | 1 | 1 | X | X |

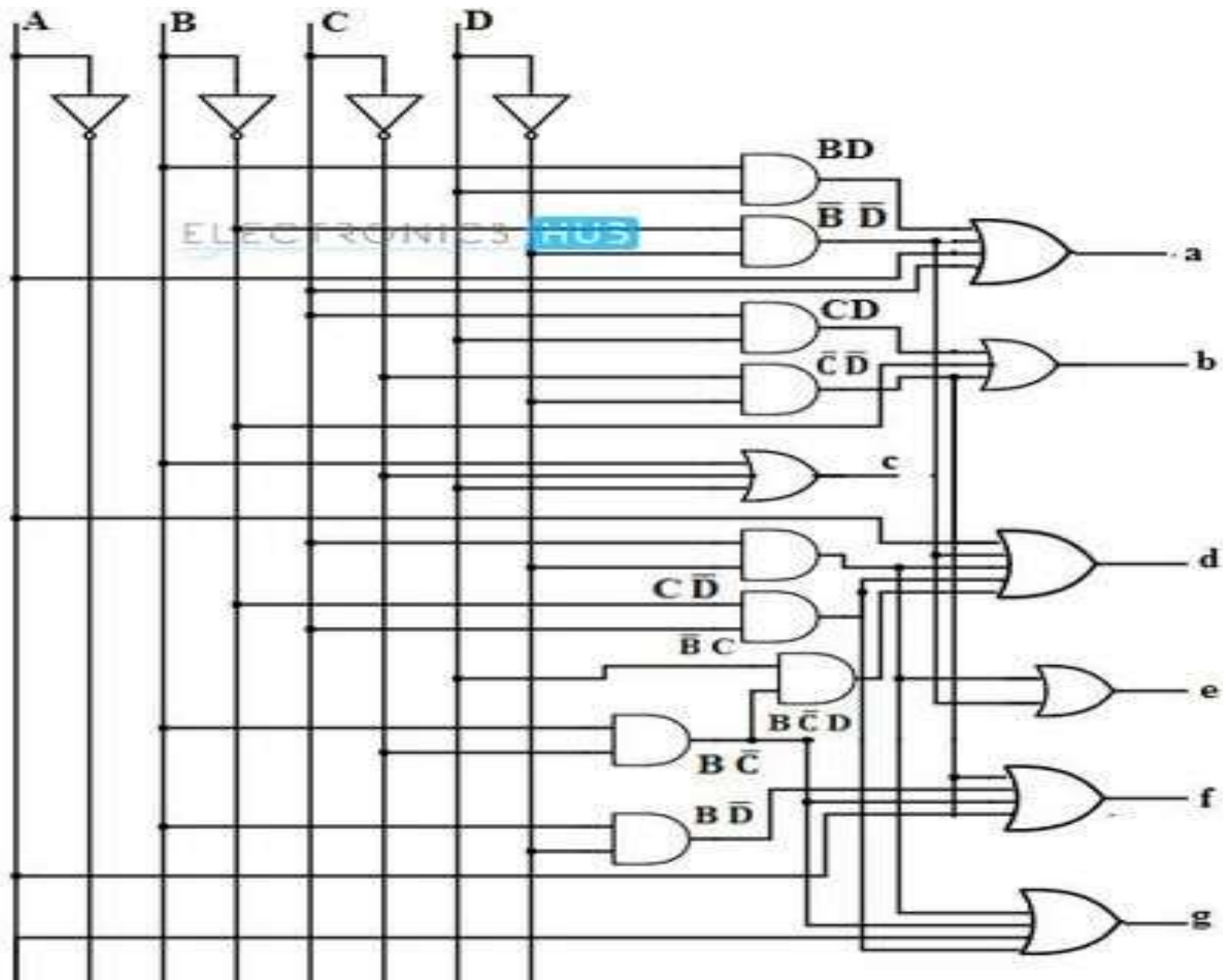FOR g: $F(A,B,C,D) = B'C + BC' + A + BD'$



Thank you