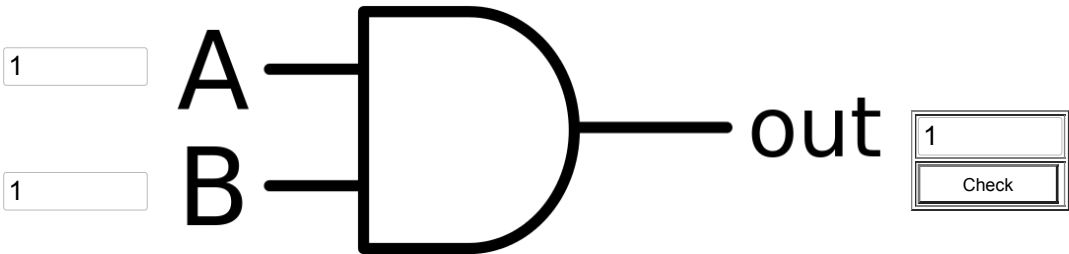


INSTRUCTIONS

Verification of truth table for AND gate



TRUTH TABLE

Print

Serial No.	A	B	Output	Remarks
1	0	0	0	Correct
2	1	0	0	Correct
3	0	1	0	Correct
4	1	1	1	Correct

Reset