



# **SATHYABAMA**

INSTITUTE OF SCIENCE AND TECHNOLOGY  
(DEEMED TO BE UNIVERSITY)

Accredited with 'A' Grade by NAAC



## **Lecture session 1\_ UNIT-3**

# **SCSA1201-FUNDAMENTALS OF DIGITAL SYSTEMS**

## **Unit-3-COMBINATIONAL LOGIC**

### **Topic 1: ADDER**

By

**V.GEETHA**

**ASSISTANT PROFESSOR/EEE**

**SATHYABAMA INSTITUTE OF SCIENCE AND TECHNOLOGY**

**CHENNAI-119**

# UNIT 3 COMBINATIONAL LOGIC

Introduction to Combinational circuits

## TOPIC 1:

- Half Adder, Full Adder - Half Subtractor, Full Subtractor
- Parallel binary Adder,-Parallel binary Subtractor

## TOPIC 2

- Carry look ahead Adder
- BCD Adder

## TOPIC 3

- Decoders
- Encoders
- Priority Encoder

## -TOPIC 4

- Multiplexers-

MUX as universal combinational modules

- Demultiplexers


## TOPIC 5

- Code convertors
- Magnitude Comparator.

# INTRODUCTION TO COMBINATIONAL CIRCUITS
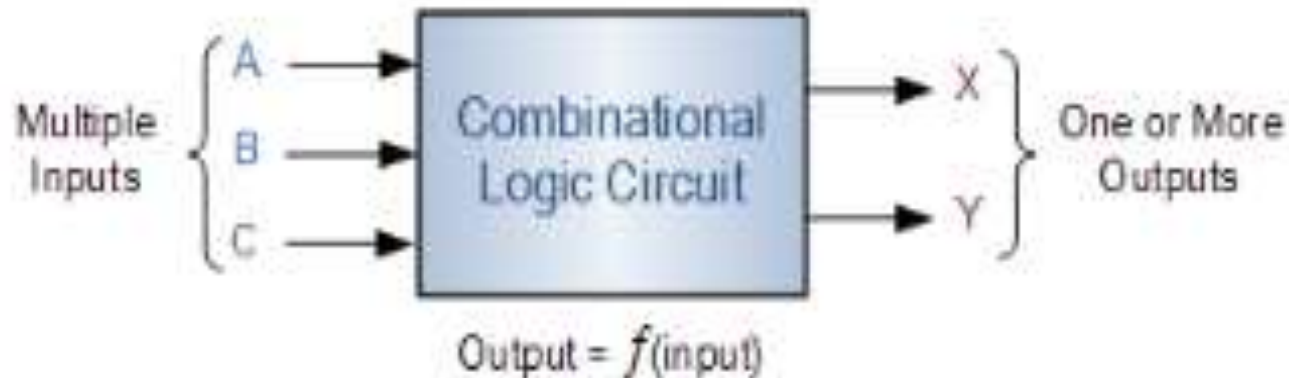
## Definition:

when logic gates are converted together to produce a specified output for a certain specified combinations of input variables, with no storage involved, the resulting circuit is called “COMBINATIONAL CIRCUIT”.



## **Design Procedure**

1. Problem definition
2. Determine required number of inputs and outputs from the specifications.
3. Assigning letters and symbols to input and output variable
4. The derivation of truth table indicating the relationship between the input and output variables
5. Obtain the simplified Boolean expressions for each output.
6. Obtain the logical diagram.

## EXAMPLE:

Design a combinational logic circuit with three input variables that will produce a logic 1 output when more than one input variables are logic 1.

No of inputs and no of outputs

inputs = 3


output = 1

K-MAP TO FIND THE RELATION BETWEEN INPUT AND OUTPUT

A	B	C	Y
0	0	0	
0	0	1	
0	1	1	1
1	0	0	
1	0	1	1
1	1	0	1
1	1	1	1


	B'C'	B'C	BC	BC'
A'	0	0	1	0
A	0	1	1	1

$$Y = AB + BC + AC$$

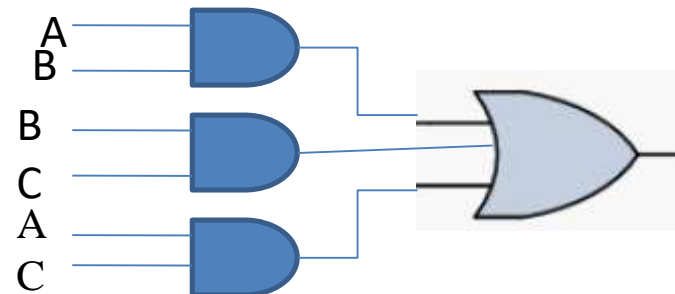

COMBINATIONAL CIRCUIT
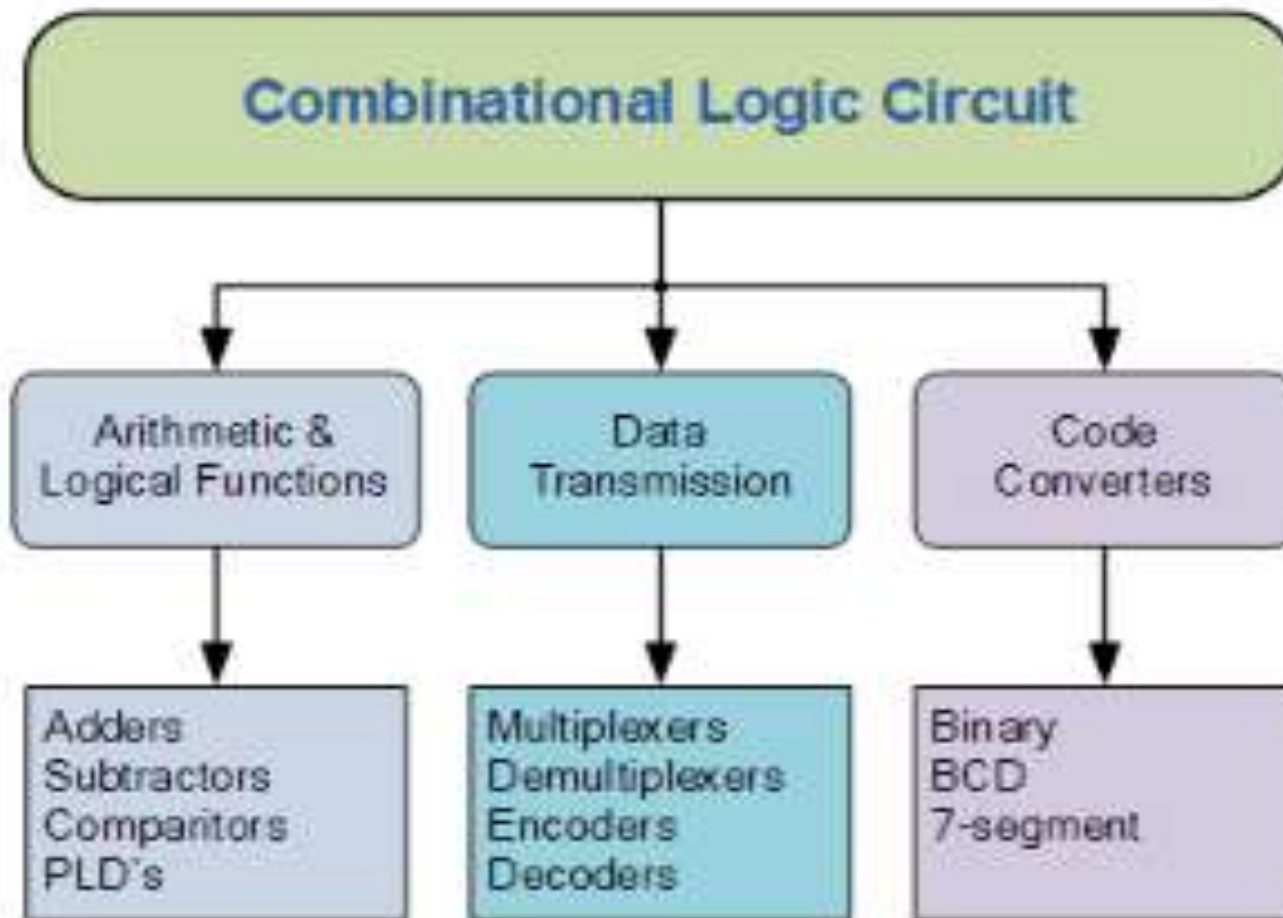
# CLASSIFICATION OF COMBINATIONAL CIRCUITS



## **What is an Adder?**

An adder is a kind of calculator that is used to add two binary numbers. When I say, calculator, I don't mean one with buttons, this one is a circuit that can be integrated with many other circuits for a wide range of applications.


There are two kinds of adders;

Half adder

Full adder
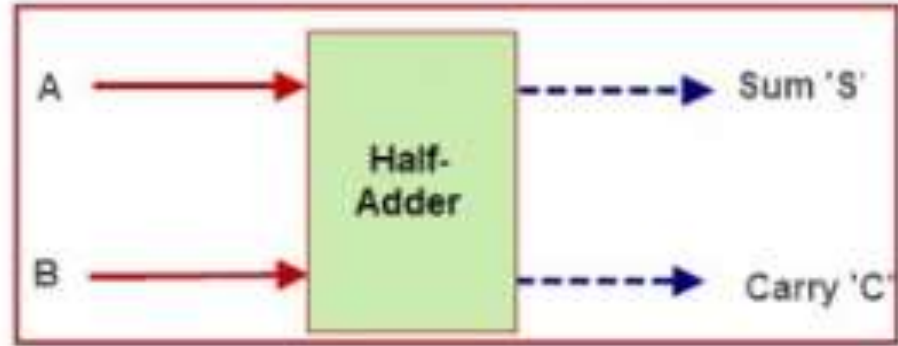
# HALF ADDER

$$\begin{aligned}0+0 &= 0 \\0+1 &= 1 \\1+0 &= 1 \\1+1 &= 10\end{aligned}$$



Half Adder

These are the least possible single-bit combinations. But the result for 1+1 is 10, the sum result must be re-written as a 2-bit output.

Thus, the equations can be written as

$$\begin{aligned}0+0 &= 00 \\0+1 &= 01 \\1+0 &= 01 \\1+1 &= 10\end{aligned}$$

A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1



A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

A \ B	0	1
0	0	1
1	1	0

$$A \cdot \overline{B} + \overline{A} \cdot B$$


AND

A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

A \ B	0	1
0	0	0
1	0	1


$$A \cdot B$$

Half Adder

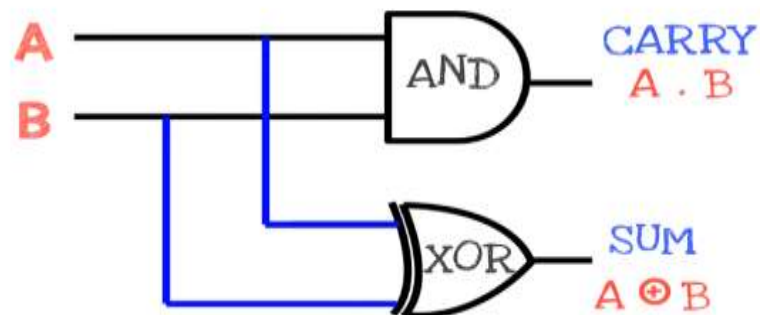
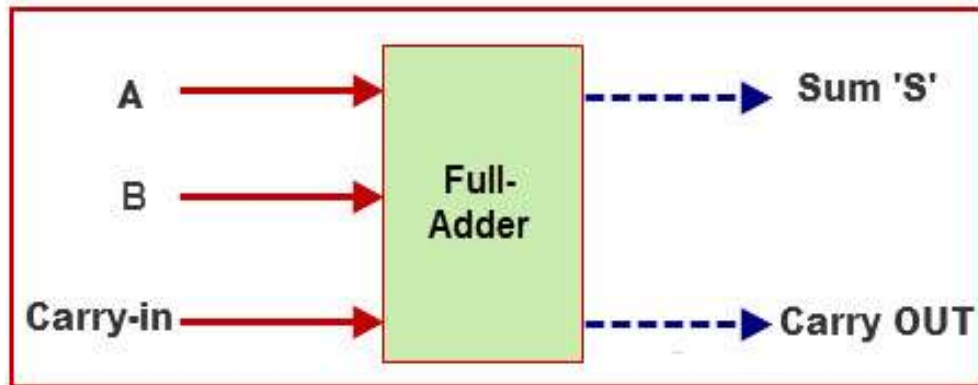
# **FULL ADDER**

The difference between a half-adder and a full-adder is that the full-adder has three inputs and two outputs, whereas half adder has only two inputs and two outputs. The first two inputs are A and B and the third input is an input carry as C-IN. When a full-adder logic is designed, you string eight of them together to create a byte-wide adder and cascade the carry bit from one adder to the next.



INPUTS			OUTPUT	
A	B	C-IN	C-OUT	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

From the above table, we can draw K-map for sum (s) and final carry ( $C_{out}$ ).

A	BC			
	00	01	11	10
0	0	1	3	2
1	1	5	7	6


**K-map for Sum (S)**

A	BC			
	00	01	11	10
0	0	1	3	2
1	4	1	7	6


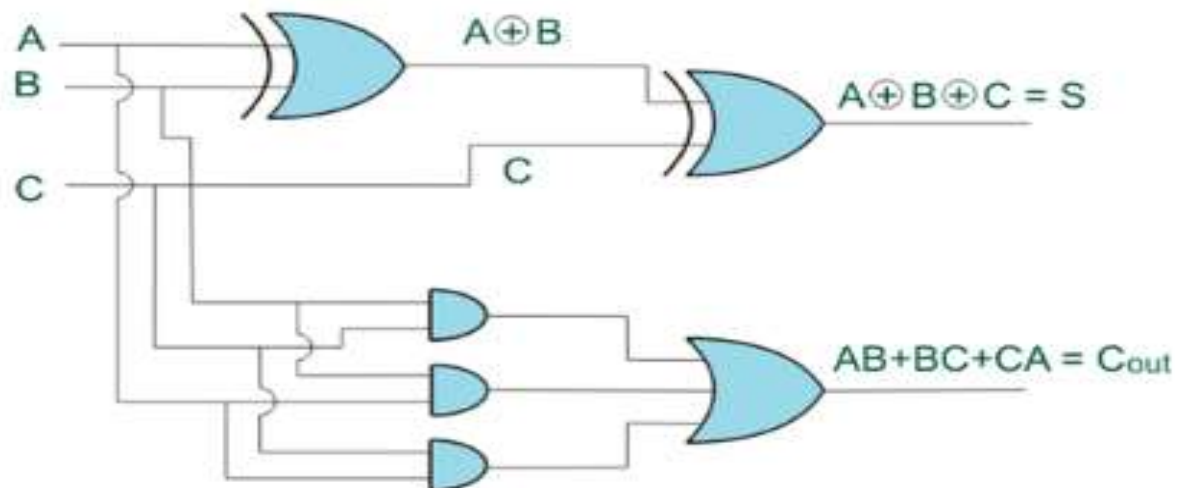
**K-map for Carry ( $C_{out}$ )**

Hence, from K-maps,

$$\begin{aligned} S &= \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}BC \\ &= C(\overline{A}\overline{B} + \overline{A}B) + \overline{C}(\overline{A}\overline{B} + \overline{A}B) \\ &= C(\overline{A}(\overline{B} + B)) + \overline{C}(\overline{A}(\overline{B} + B)) \\ &= C(\overline{A}) + \overline{C}(\overline{A}) = A \oplus B \oplus C. \end{aligned}$$


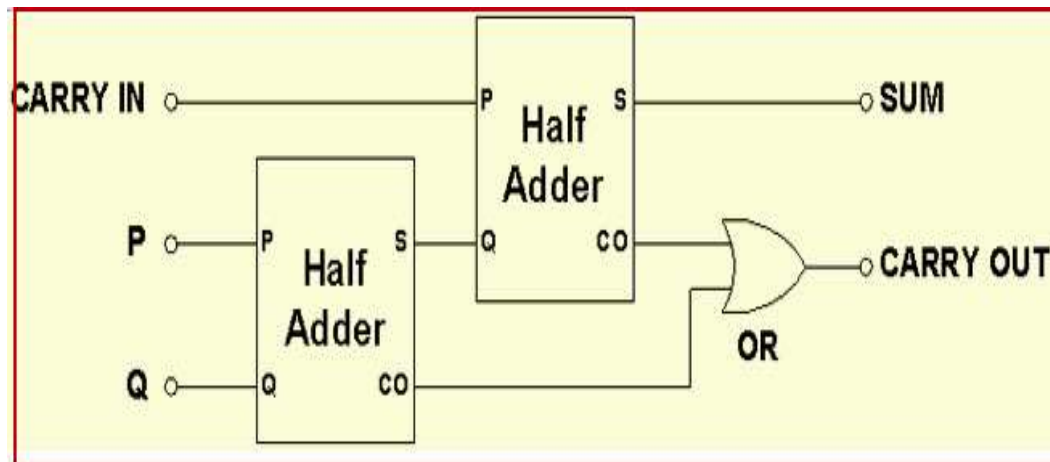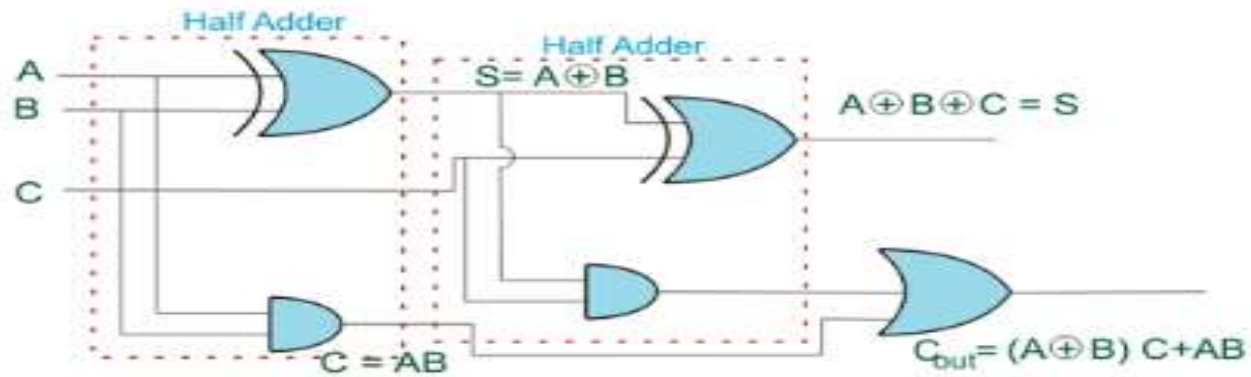
$$\begin{aligned}
 C_{out} &= \overline{A}BC + A\overline{B}C + ABC\overline{C} + ABC \\
 &= (\overline{A}B + A\overline{B})C + AB(\overline{C} + C) \\
 &= (A \oplus B) \cdot C + AB.
 \end{aligned}$$



*Thank you*