



# **SATHYABAMA**

INSTITUTE OF SCIENCE AND TECHNOLOGY  
(DEEMED TO BE UNIVERSITY)

Accredited with 'A' Grade by NAAC



## **Lecture session 2\_ UNIT-3**

### **Unit-3-COMBINATIONAL LOGIC**

### **SUBTRACTORS and PARALLEL ADDER**

**By**

**V.GEETHA**

**ASSISTANT PROFESSOR/EEE**

**SATHYABAMA INSTITUTE OF SCIENCE AND TECHNOLOGY**

**CHENNAI-119**

## Half Subtractor-

- Half Subtractor is a combinational logic circuit.
- It is used for the purpose of subtracting two single bit numbers.
- It contains 2 inputs and 2 outputs (difference and borrow).



### Step-01:

Identify the input and output variables-

- Input variables = A, B (either 0 or 1)
- Output variables = D, b where D = Difference and b = borrow

## **Step-02:**

Draw the truth table-


Inputs		Outputs	
A	B	D (Difference)	b (Borrow)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

**Truth Table**

### Step-03:


Draw K-maps using the above truth table and determine the simplified Boolean expressions-

For D:

 

$$D = A \oplus B$$

For b:

 


$$b = \bar{A}.B$$

K Maps
 
#### Step-04:

Draw the logic diagram.

The implementation of half subtractor using 1 XOR gate, 1 NOT gate and 1 AND gate is as shown below-



**Half Subtractor Logic Diagram**


## Limitation of Half Subtractor-

- Half subtractors do not take into account "Borrow-in" from the previous circuit.
- This is a major drawback of half subtractors.
- This is because real time scenarios involve subtracting the multiple number of bits which can not be accomplished using half subtractors.

To overcome this drawback, Full Subtractor comes into play.
 
## Full Subtractor-

- Full Subtractor is a combinational logic circuit.
- It is used for the purpose of subtracting two single bit numbers.
- It also takes into consideration borrow of the lower significant stage.
- Thus, full subtractor has the ability to perform the subtraction of three bits.
- Full subtractor contains 3 inputs and 2 outputs (Difference and Borrow) as shown-



## Step-01:

Identify the input and output variables-

- Input variables = A, B,  $B_{in}$  (either 0 or 1)
- Output variables = D,  $B_{out}$  where D = Difference and  $B_{out}$  = Borrow

## Step-02:

Draw the truth table-

Inputs			Outputs	
A	B	$B_{in}$	$B_{out}$ (Borrow)	D (Difference)
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

**Truth Table**

### Step-03:

Draw K-maps using the above truth table and determine the simplified Boolean expressions-

For D:

		$BB_{in}$	$\bar{B}\bar{B}_{in}$	$\bar{B}B_{in}$	$BB_{in}$	$B\bar{B}_{in}$
		$\bar{A}$		1		1
A	$\bar{A}$		1		1	
	A	1			1	

$$D = A \oplus B \oplus B_{in}$$

For  $B_{in}$ :

		$BB_{in}$	$\bar{B}\bar{B}_{in}$	$\bar{B}B_{in}$	$BB_{in}$	$B\bar{B}_{in}$
		$\bar{A}$		1	1	1
A	$\bar{A}$			1	1	1
	A				1	


$$B_{out} = \bar{A}B + (\bar{A} + B)B_{in}$$


 
#### Step-04:

Draw the logic diagram.

The implementation of full adder using 1 XOR gate, 3 AND gates, 1 NOT gate and 1 OR gate is as shown below-



**Full Subtractor Logic Diagram**

## Simplification of D:


$$= A\bar{B}\bar{B}_{in} + \bar{A}\bar{B}B_{in} + AB\bar{B}_{in} + \bar{A}B\bar{B}_{in}$$

$$= B_{in}(A\bar{B} + \bar{A}\bar{B}) + \bar{B}_{in}(A\bar{B} + \bar{A}B)$$

$$= B_{in}(A \odot B) + \bar{B}_{in}(A \oplus B)$$

$$= B_{in}(A \oplus B) + \bar{B}_{in}(A \oplus B)$$

$$= B_{in} \oplus A \oplus B.$$

 

Full subtractor with two half subtractor,

$$B_{out} = \bar{A}B_{in} + \bar{A}B + BB_{in}$$

$$= \bar{A}B + \bar{A}B_{in}(B + \bar{B}) + BB_{in}(A + \bar{A})$$


$$= \bar{A}B + \bar{A}B_{in}B + \bar{A}\bar{B}B_{in} + AB B_{in} + \bar{A}B B_{in}$$

$$= \bar{A}B + \bar{A}B_{in}B + \bar{A}\bar{B}B_{in} + AB B_{in}$$

$$= \bar{A}B(1 + B_{in}) + (\bar{A}\bar{B} + AB)B_{in}$$

$$= \bar{A}B + (A \odot B)B_{in}$$
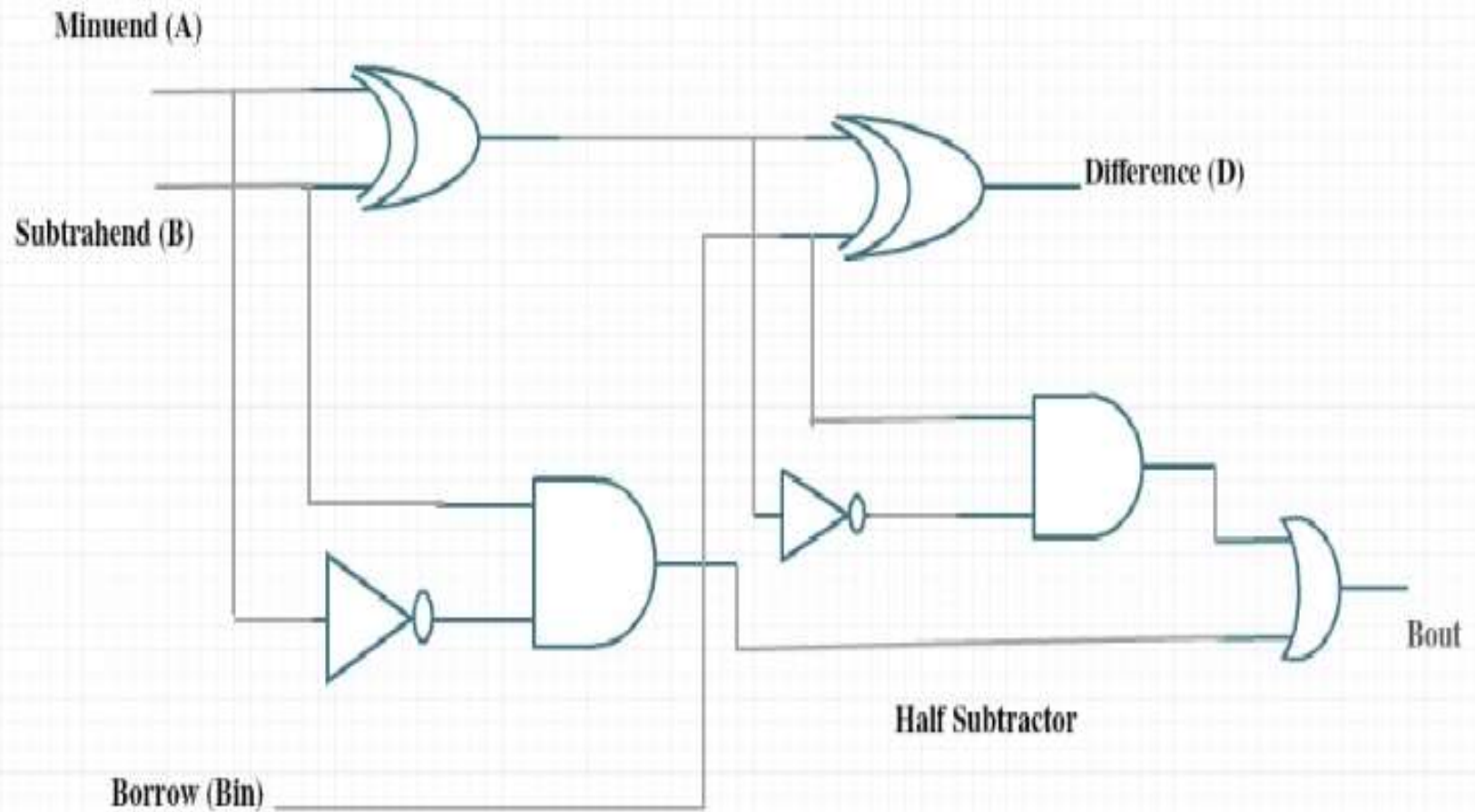
$$= \bar{A}B + \overline{(A \oplus B)}B_{in}$$




Half Subtractor

Half Subtractor

Full Subtractor
 
### 3. Binary Adder (Asynchronous Ripple-Carry Adder)



- A binary adder is a digital circuit that produces the *arithmetic sum of two binary numbers*.
- A binary adder can be constructed with *full adders connected in cascade* with the output carry from each full adder connected to the input carry of the next full adder in the chain.
- The *four-bit adder* is a typical example of a *standard component*. It can be used in many application involving arithmetic operations.




*Four-bit Adder (Ripple Carry Adder)*

1. Design a 4 bit parallel adder using full adders.

\* 4 Full adders.

 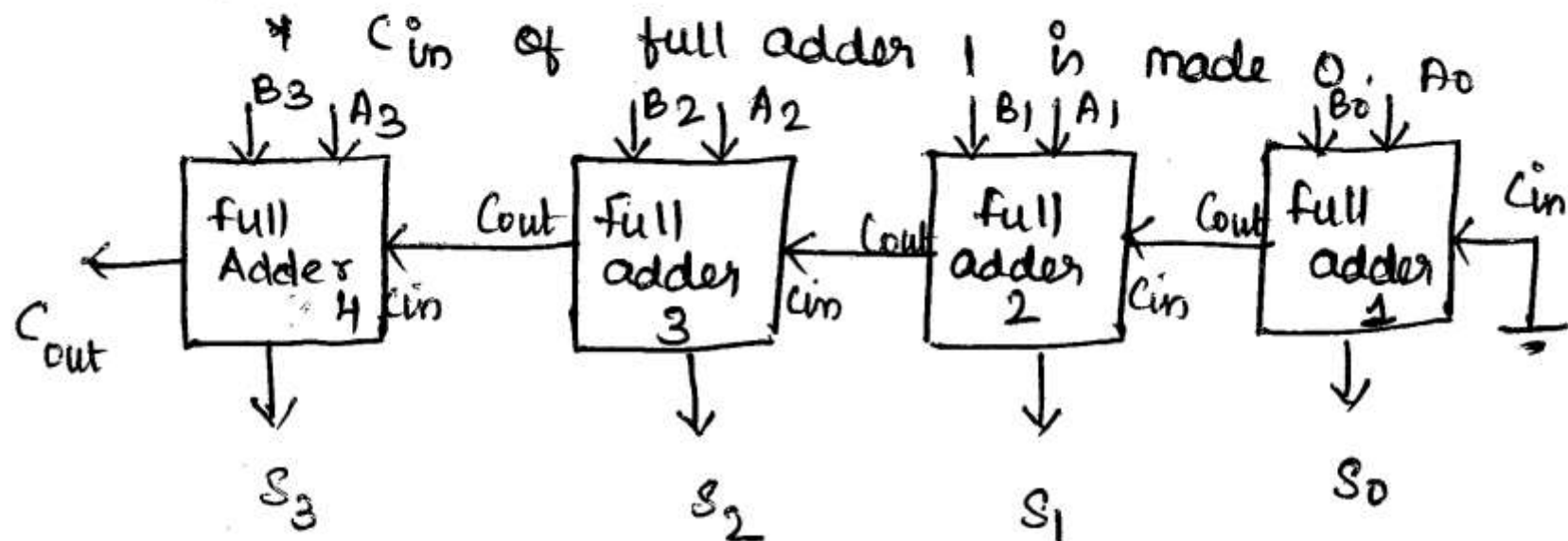

 2. Design a 8 bit adder using two four bit adder.




## Parallel subtractor

Subtraction of binary numbers can be done most conveniently by means of Complements.

Subtraction of A and B can be done by taking 2's complement of B and adding it with A.

2's Complement is done by taking 1's Complement and adding 1 to 1's Complement number.

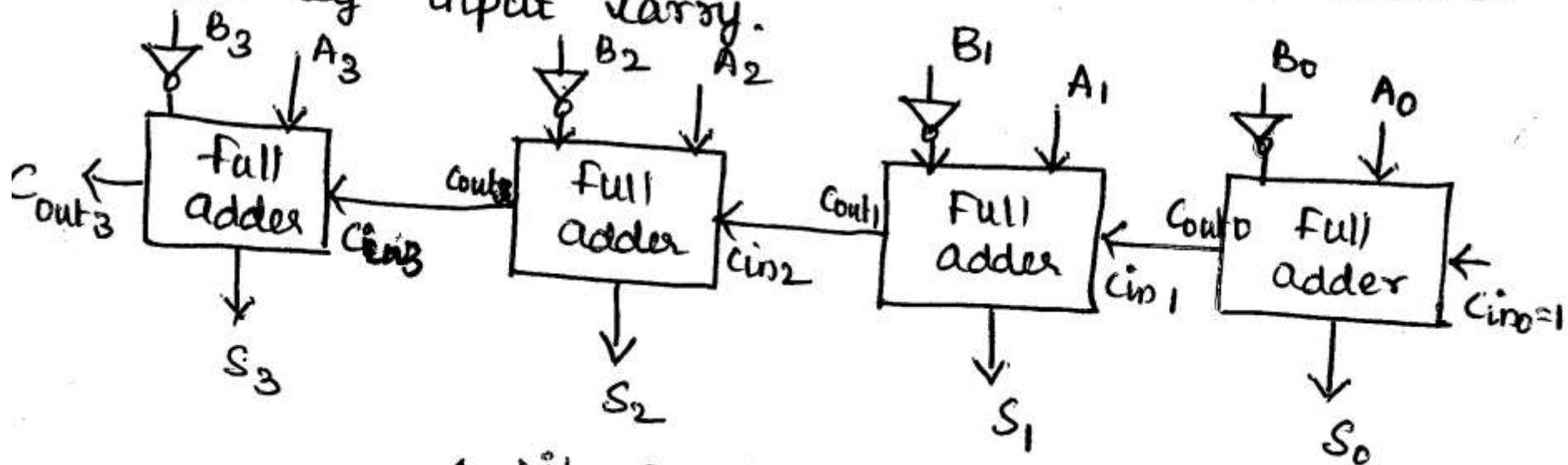1's Complement is done by taking inversion of the number. Here 1 is added to the complemented number by input carry.




4-bit parallel subtractor.


 
## 5. Binary Adder-Subtractor

- The addition and subtraction operations can be combined into one circuit with one common binary adder by including an *exclusive-OR* gate with each full-adder.



The mode input  $M$  controls the operation as the following:

- ( $M = 0$  → adder.
- $M = 1$  → subtractor.
- Each **XOR** gate receives  $M$  signal and  $B$ 
  - When  $M = 0$  then  $B \oplus 0 = B$  and the carry =  $0$ , then the circuit performs the operation  $A + B$ .
  - When  $M = 1$  then  $B \oplus 1 = \bar{B}$  and the carry =  $1$ , then the circuit performs the operation  $A - B$ .
- The **exclusive-OR** with output  $V$  is for detecting an overflow.

## CARRY PROPAGATION DELAY

$A + B$

( $A = 1011$ ) and ( $B = 0011$ )


Subscript $i$	3	2	1	0	
Input Carry	0	1	1	0	$C_i$
$A$	1	0	1	1	$A_i$
+					
$B$	0	0	1	1	$B_i$
Sum	1	1	1	0	$S_i$
Output Carry	0	0	1	1	$C_{i+1}$

$C_0 = 0$

The carry propagation time is an important attribute of the adder because it limits the speed with which two numbers are added.

To reduce the carry propagation delay time:

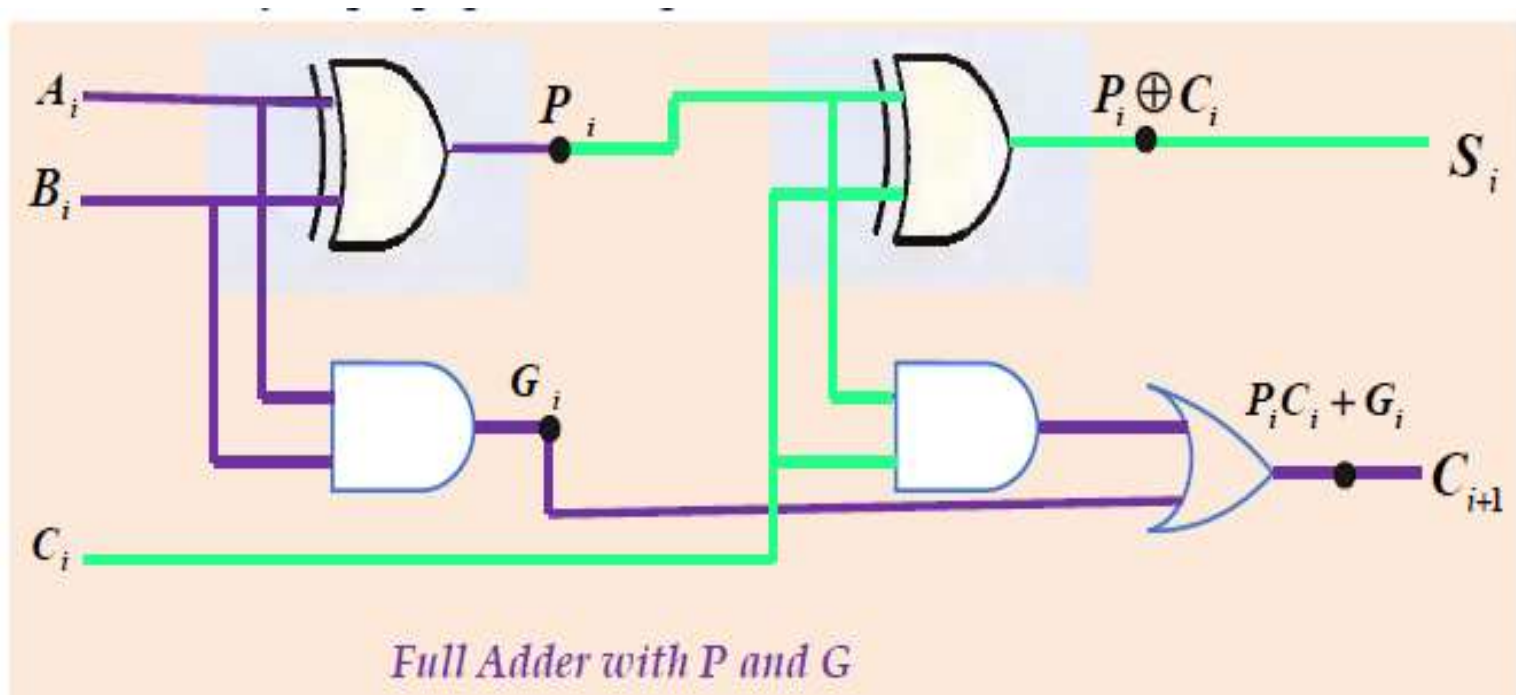- 1) Employ faster gates with reduced delays.
- 2) Employ the principle of Carry Look ahead Logic.



**Proof:** (using carry lookahead logic)

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

The output sum and carry are:


$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

- ✓  $G_i$ -called a **carry generate**, and it produces a carry of  $1$  when both  $A_i$  and  $B_i$  are  $1$ .
- ✓  $P_i$ -called a **carry propagate**, it determines whether a carry into stage  $i$  will propagate into stage  $i + 1$ .
- ✓ The *Boolean function* for the carry outputs of each stage and substitute the value of each  $C_i$  from the previous equations:


$$\left\{ \begin{array}{l} C_0 = \text{input carry} \\ C_1 = G_0 + P_0 C_0 \\ C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) \\ \quad = G_1 + P_1 G_0 + P_1 P_0 C_0 \\ C_3 = G_2 + P_2 C_2 = G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0) \\ \quad = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \end{array} \right\}$$

 - The three Boolean functions  $C_1$ ,  $C_2$  and  $C_3$  are implemented in the **carry lookahead generator**.



The two level-circuit for the output carry  $C_4$  is not shown, it can be easily derived by the equation.

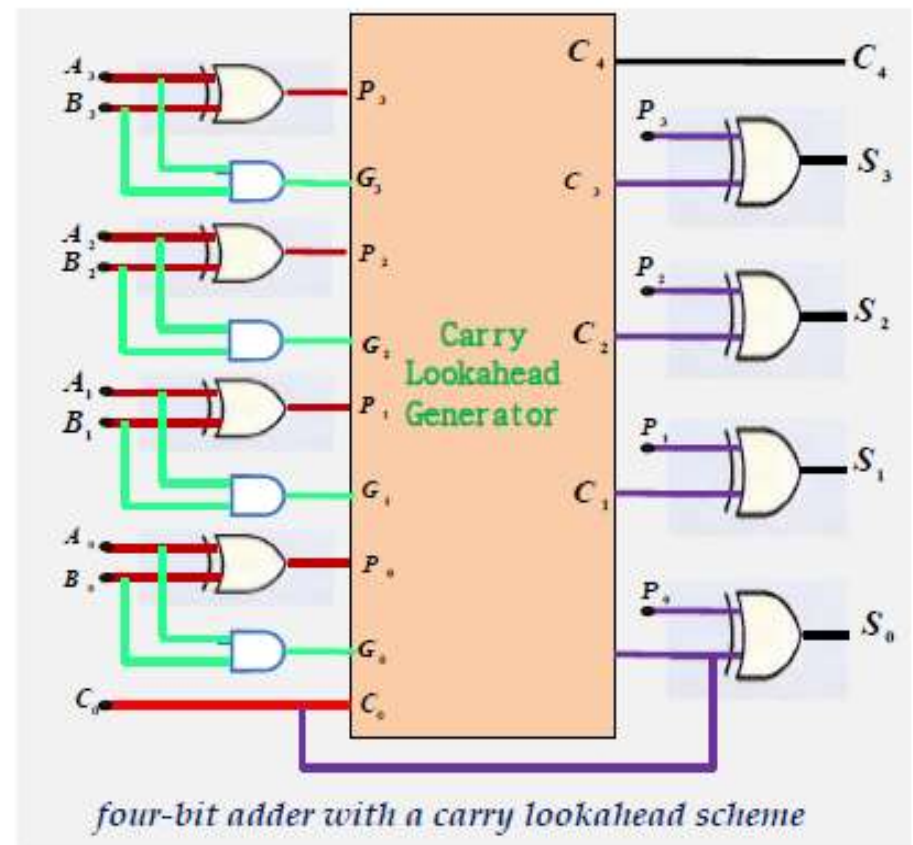- $C_3$  does not have to wait for  $C_2$  and  $C_1$  to propagate, in fact  $C_3$  is propagated at the same time as  $C_1$  and  $C_2$ .



Thank you